

Serial Data Transmitter

Presented to: Dr. Mohamed El-Banna

Dr. Nayera Sadek

Eng. Khaled Essam

Eng. Mostafa Ayesh

By: Mostafa Mahmoud Khalil Hassan

VHDL Code:

Library IEEE;

Use IEEE.STD_LOGIC_1164.ALL;

Use IEEE.STD_LOGIC_UNSIGNED.ALL;

Entity transmitter is

```
    Port ( din          : in STD_LOGIC_VECTOR (6 downto 0);      -- input data that will be sent
          start_transmit : in STD_LOGIC;                          -- enable sending
          clk            : in STD_LOGIC;
          serial_out     : BUFFER STD_LOGIC);                     -- the sent data
```

End transmitter ;

Architecture Behavior of transmitter is

```
    Signal parity_bit   : STD_LOGIC;
    Signal da           : STD_LOGIC_VECTOR (8 downto 0);
    Signal m             : STD_LOGIC_vector (1 downto 0) := "00";
    -- That is a counter to not to load the same data again.
```

Begin

```
    parity_bit <= din(0) xor din(1) xor din(2) xor din(3) xor din(4) xor din(5) xor din(6) ;
```

Process

Begin

```
    Wait until (clk'EVENT AND clk='1') ;
    if start_transmit='1' then
        if (m = "00") then
            da (8 downto 0) <= '1' & parity_bit & din (6 downto 0);
            serial_out <= '1';
            m <= "01" ;
        elsif (m = "01") then
            Genbits: FOR i IN 0 To 7 LOOP                -- shifting circuit
                da (i) <= da(i+1);
            End LOOP;
            serial_out <= da (0);
            da (8) <= '0';
        End if;
    elsif start_transmit = '0' then
        m <= "00";
        da <= "000000000" ;
        serial_out <= '0';
```

End if;


End process;

End Behavioral;


The steps of the design:

The simulation


1- When Start_transmit = 0 .

 

 
2- When start transmit =1 , it send start bit and clk is 1




 - 3- When start transmit =1 , it send all data bits including the parity_bit and the stop bit. And clk is 0 . it will wait for the rising edge.




 - 4- When start transmit = 1 , clk = 1 , start shifting 1 bit then clk change to 0 (will wait for the next rising edge to shift the other bit etc.)



 

 all din are sent so it will back to 0000000000



block diagram :

